

Lovely Professional University  
Continuous Assessment-1  
Computer Organization and Design  
Set-A

M.M: 30

Date of submission: 25<sup>th</sup> Sept'21

Q.1 Design a circuit that would be able to shift bits but also store them for a duration of time. Explain what are the technicalities of such a circuit. [5 marks]

Q.2 As a designer you have to obtain results using registers to following equation:

$$R3 \leftarrow R1 + R2$$

What would be an appropriate circuit to do so and why? [5 marks]

Q.3 Design a bus system that can support 4 registers of 2 bits each. Explain why you created the bus in this method. Also explain how to gather data from this bus back into register. [10 Marks]

Q.4 A hardware implementation is required for executing the following equations, draw proper diagrams to complete your results. [5 marks]

1-  $x + y + z + a.b : R3 \leftarrow R4 - R5$

2-  $a.c.b + d : R3 \leftarrow R4 + R6$

Q.5 Explain with examples [5 marks]

1- Shift left

2- Shift right

3- Circular shift

4- Computer organization